

# Digital Design and Computer Organisation Laboratory

UE22CS251A

3rd Semester, Academic Year 2023-24

Date: 04/09/2024

Name: Keerthan P.V.	SRN: PES2UG23CS272	Section 3E
------------------------	-----------------------	---------------

Week:4

Program Number:1

TITLE:

**WRITE A VERILOG PROGRAM TO MODEL A 2: 1 MULTIPLEXER. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH TABLE**

## I. Verilog Code and Test Bench Code

1.mux.v

```
module mux2 (  
    input wire i0, i1, j,  
    output wire o  
);  
    assign o = (j == 0) ? i0 : i1;  
endmodule
```

## 2.mux\_tb.v


```
module TB;
  reg A, B, S;
  wire X;
  mux2 newMUX(.i0(A), .i1(B), .j(S), .o(X));

  initial begin
    S = 1'b0; A = 1'b0; B = 1'b0;
    #5 S = 1'b0; A = 1'b0; B = 1'b1;
    #5 S = 1'b0; A = 1'b1; B = 1'b0;
    #5 S = 1'b0; A = 1'b1; B = 1'b1;
    #5 S = 1'b1; A = 1'b0; B = 1'b0;
    #5 S = 1'b1; A = 1'b0; B = 1'b1;
    #5 S = 1'b1; A = 1'b1; B = 1'b0;
    #5 S = 1'b1; A = 1'b1; B = 1'b1;
  end
  initial begin
    $monitor("Time = %0t: A = %b, B = %b, S = %b, X = %b", $time, A, B, S, X);
  end
  initial begin
    $dumpfile("MUX2_test.vcd");
    $dumpvars(0,TB);
  end
endmodule
```

## II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>vvp test
VCD info: dumpfile MUX2_test.vcd opened for output.
Time = 0: A = 0, B = 0, S = 0, X = 0
Time = 5: A = 0, B = 1, S = 0, X = 0
Time = 10: A = 1, B = 0, S = 0, X = 1
Time = 15: A = 1, B = 1, S = 0, X = 1
Time = 20: A = 0, B = 0, S = 1, X = 0
Time = 25: A = 0, B = 1, S = 1, X = 1
Time = 30: A = 1, B = 0, S = 1, X = 0
Time = 35: A = 1, B = 1, S = 1, X = 1
```

### III. GTKWAVE Screenshot

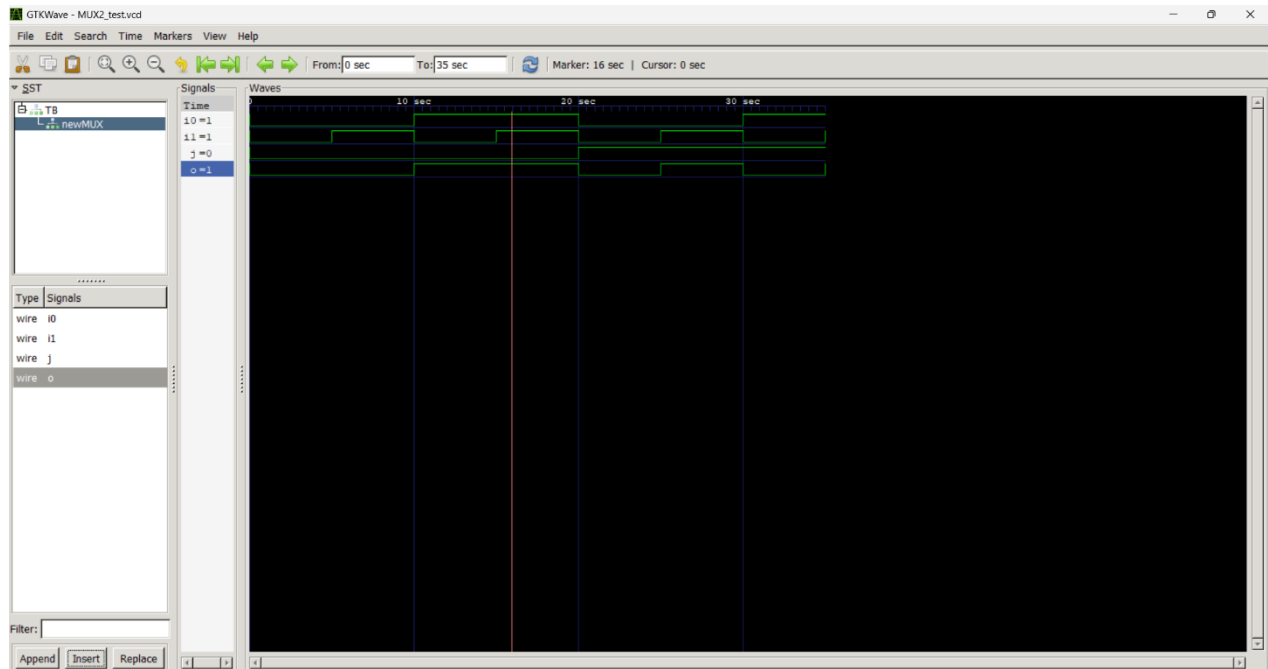

Week:4

Program Number:2

TITLE :

**WRITE A VERILOG PROGRAM TO MODEL A 4:1 MULTIPLEXER USING 2:1 MULTIPLEXERS. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH TABLE**

## I. Verilog Code and Test Bench Code

### 1.mux4.v

```
module mux4(input wire [0:3] i, input wire j0, j1, output wire o);
    wire [0:1] s;
    assign s = j1 ? {j0, 1'b1} : {j0, 1'b0};

    assign o = (s == 2'b00) ? i[0] :
               (s == 2'b01) ? i[1] :
               (s == 2'b10) ? i[2] :
               i[3];
endmodule
```


### 2.mux4\_tb.v

```
module TB;
    reg [0:3] ii;
    reg s0; reg s1;
    wire yy;
    mux4 newMUX(.i(ii), .j0(s0), .j1(s1), .o(yy));
    initial begin
        ii = 4'b0000; s0=1'b0; s1=1'b0;
        #5      ii = 4'b1000; s0=1'b0; s1=1'b0;
        #5      ii = 4'b0000; s0=1'b0; s1=1'b1;
        #5      ii = 4'b0100; s0=1'b0; s1=1'b1;
        #5      ii = 4'b0000; s0=1'b1; s1=1'b0;
        #5      ii = 4'b0010; s0=1'b1; s1=1'b0;
        #5      ii = 4'b0000; s0=1'b1; s1=1'b1;
        #5      ii = 4'b0001; s0=1'b1; s1=1'b1;
    end
    initial begin
        $monitor("Time = %0t: ii = %b, s0 = %b, s1 = %b, yy = %b", $time, ii, s0, s1, yy);
    end
    initial begin
        $dumpfile("MUX4_test.vcd");
        $dumpvars(0, TB);
    end
endmodule
```

## II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>vvp test
VCD info: dumpfile MUX4_test.vcd opened for output.
Time = 0: ii = 0000, s0 = 0, s1 = 0, yy = 0
Time = 5: ii = 1000, s0 = 0, s1 = 0, yy = 1
Time = 10: ii = 0000, s0 = 0, s1 = 1, yy = 0
Time = 15: ii = 0100, s0 = 0, s1 = 1, yy = 1
Time = 20: ii = 0000, s0 = 1, s1 = 0, yy = 0
Time = 25: ii = 0010, s0 = 1, s1 = 0, yy = 1
Time = 30: ii = 0000, s0 = 1, s1 = 1, yy = 0
Time = 35: ii = 0001, s0 = 1, s1 = 1, yy = 1
```

## III. GTKWAVE Screenshot

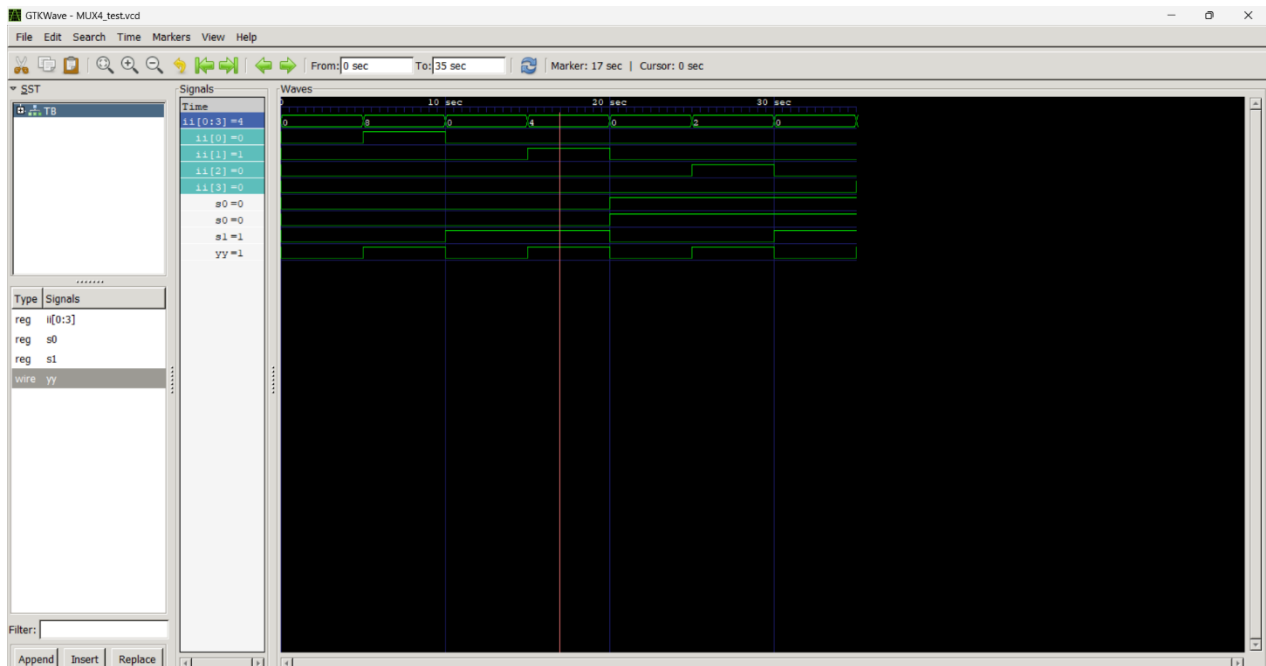

Week:4

Program Number:3

TITLE:

**WRITE A VERILOG PROGRAM TO MODEL A 1:2 DEMULTIPLEXER.GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH TABLE**

## I. Verilog Code and Test Bench Code

### 1.demux21.v

```
module demux2 (  
    input wire in, sel,  
    output wire y0, y1  
);  
    assign y0 = (sel == 0) ? in : 0;  
    assign y1 = (sel == 1) ? in : 0;  
  
endmodule
```


### 2.demux21\_tb.v

```
module TB;  
    reg i,s;  
    wire y0,y1;  
    demux2 newMUX(.in(i), .sel(s), .y0(y0), .y1(y1));  
  
    initial begin  
        i = 1'b0; s = 1'b0;  
        #5 i = 1'b0; s = 1'b1;  
        #5 i = 1'b1; s = 1'b0;  
        #5 i = 1'b1; s = 1'b1;  
    end  
    initial begin  
        $monitor("Time = %0t: in = %b, sel = %b, y0 = %b, y1 = %b", $time, i, s, y0, y1);  
    end  
    initial begin  
        $dumpfile("DEMUX2_test.vcd");  
        $dumpvars(0,TB);  
    end  
endmodule
```

## II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>vvp test
VCD info: dumpfile DEMUX2_test.vcd opened for output.
Time = 0: in = 0, sel = 0, y0 = 0, y1 = 0
Time = 5: in = 0, sel = 1, y0 = 0, y1 = 0
Time = 10: in = 1, sel = 0, y0 = 1, y1 = 0
Time = 15: in = 1, sel = 1, y0 = 0, y1 = 1
```

## III. GTKWAVE Screenshot

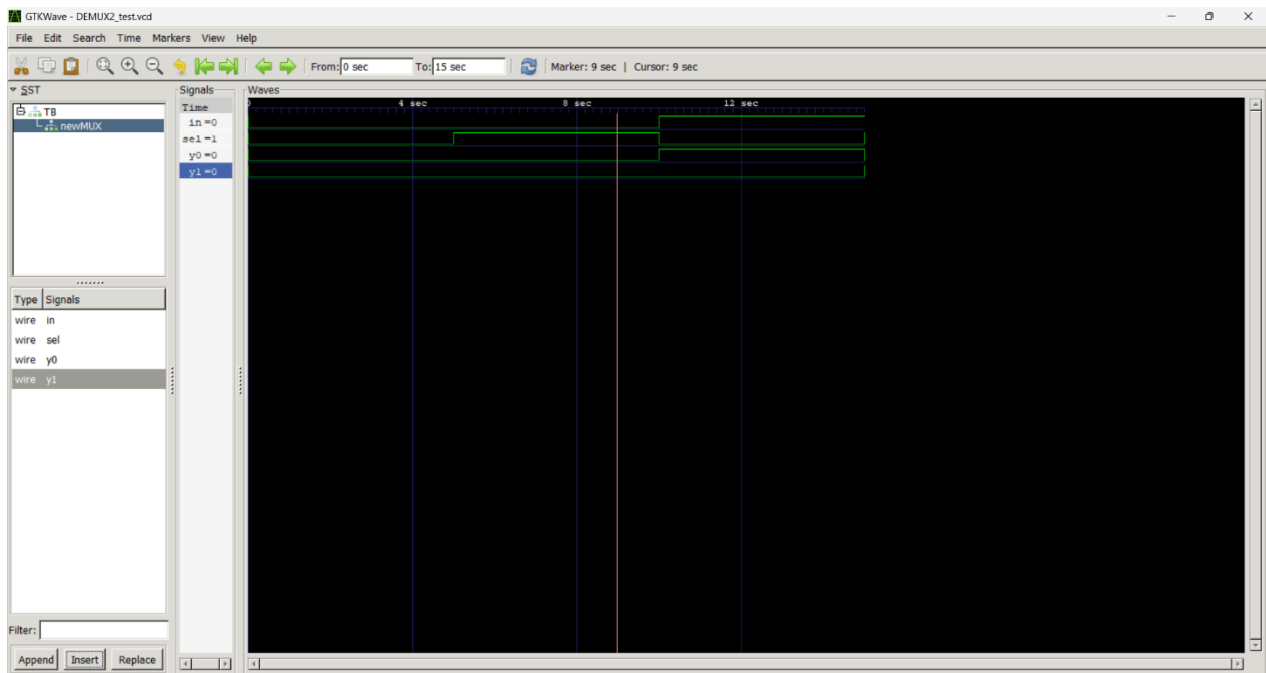


Week:4

Program Number:4

TITLE:

 **WRITE A VERILOG PROGRAM TO MODEL THE GIVEN CIRCUIT  
3.GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING  
GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH  
TABLE**



## I. Verilog Code and Test Bench Code

### 1.circuit4.v

```
module fa(input wire i0,i1,cin,output wire sum, cout);
wire t0,t1,t2;
xor3 _i0 (i0,i1,cin,sum);
and2 _i1 (i0,i1,t0);
and2 _i2 (i1,cin,t1);
and2 _i3 (cin,i0,t2);
or3 _i4 (t0,t1,t2,cout);
endmodule

module circuit3(input wire [0:2] i1, input wire i2, output wire sum1, cout1);
wire x1,x2;
fa fa_1(i1[0],i1[1],i1[2],x1,x2);
fa fa_2(x1,x2,i2,sum1,cout1);
endmodule
```



## 2.circuit4\_tb.v

```
`define TESTVECS 6

module tb;
  reg [2:0] i1;
  reg i2;
  wire sum1,cout1;

  reg [3:0] test_vecs [0:('TESTVECS-1)];
  integer i;
  initial begin
    $dumpfile("circuit3.vcd");
    $dumpvars(0,tb);
  end


  initial begin
    test_vecs[0][3:1] = 3'b000;test_vecs[0][0:0] = 1'b0;
    test_vecs[1][3:1] = 3'b001;test_vecs[1][0:0] = 1'b1;
    test_vecs[2][3:1] = 3'b010;test_vecs[2][0:0] = 1'b0;
    test_vecs[3][3:1] = 3'b011;test_vecs[3][0:0] = 1'b1;
  end
  initial begin
    $monitor("Time = %0t: i1 = %b, i2 = %b, sum1 = %b, cout1 = %b", $time, i1, i2, sum1, cout1);
  end
  initial {i1, i2} = 0;
  circuit3 circuit3_0 (i1,i2,sum1, cout1);
  initial begin
    for(i=0;i<'TESTVECS;i=i+1)
      begin #10 {i1,i2}=test_vecs[i];
    end
  end

end
endmodule
```

## II. Verilog VVP Output Screen Shot

```
Time = 0: i1 = 000, i2 = 0, sum1 = 0, cout1 = 0
Time = 20: i1 = 001, i2 = 1, sum1 = 0, cout1 = 1
Time = 30: i1 = 010, i2 = 0, sum1 = 1, cout1 = 0
Time = 40: i1 = 011, i2 = 1, sum1 = 0, cout1 = 1
Time = 50: i1 = xxx, i2 = x, sum1 = x, cout1 = x
```

### III. GTKWAVE Screenshot

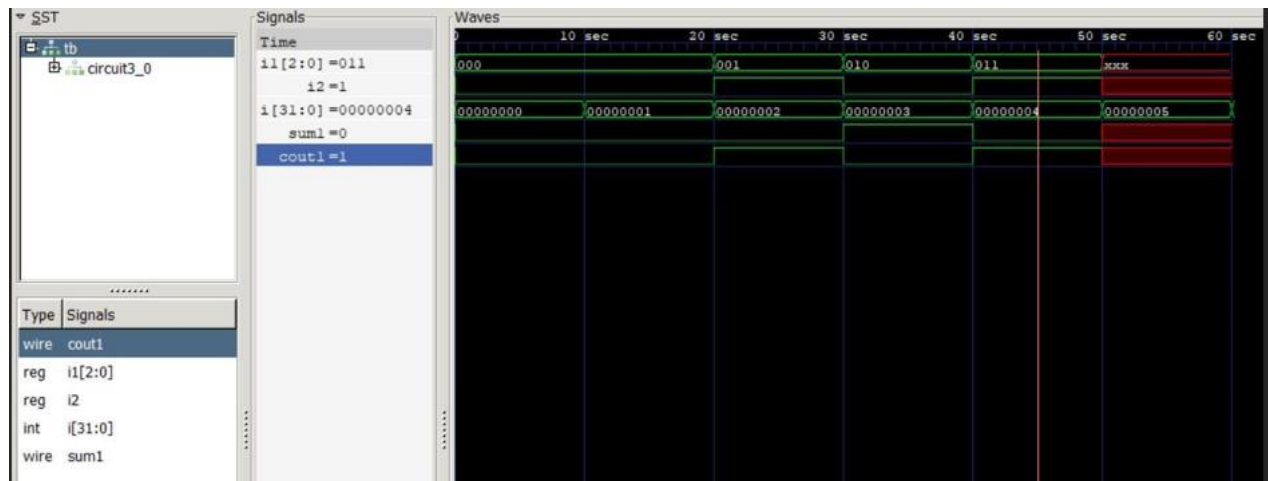


Week:4

Program Number:5

TITLE:

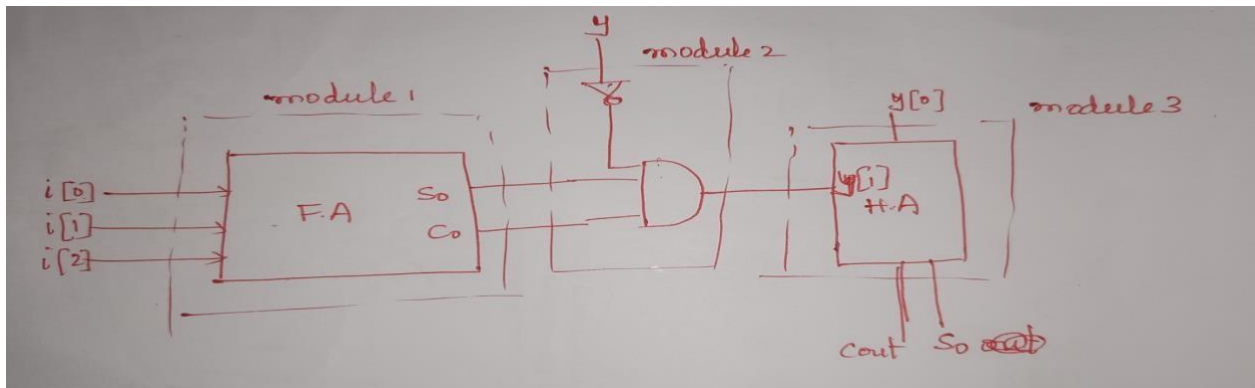WRITE A VERILOG PROGRAM TO MODEL THE GIVEN CIRCUIT  
4.GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING  
GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE TRUTH  
TABLE



## I. Verilog Code and Test Bench Code

### 1.circuit5.v

```
module fa (input wire i0, i1, cin, output wire sum, cout);  wire t0, t1, t2;
  xor3 _i0 (i0, i1, cin, sum);
  and2 _i1 (i0, i1, t0);
  and2 _i2 (i1, cin, t1);
  and2 _i3 (cin, i0, t2);
  or3 _i4 (t0, t1, t2, cout);
endmodule

module circuit3 (input wire [0:2] i1, input wire i2, output wire sum1, cout1);
  wire x1, x2;
  fa fa_1(i1[0], i1[1], i1[2], x1, x2);
  fa fa_2(x1, x2, i2, sum1, cout1);
endmodule
```

## 2.circuit5\_tb.v

```
define TESTVECS 10

module tb;
  reg [2:0] i1;
  reg y,y0;
  wire s0,cout;


  reg [4:0] test_vecs [0:(`TESTVECS-1)];
  integer i;
  initial begin
    $dumpfile("circuit4.vcd");
    $dumpvars(0,tb);
  end

  initial begin
    test_vecs[0][4:2] = 3'b000;test_vecs[0][1:1] = 1'b0;test_vecs[0][0:0] = 1'b0;
    test_vecs[1][4:2] = 3'b000;test_vecs[1][1:1] = 1'b1;test_vecs[1][0:0] = 1'b1;
    test_vecs[2][4:2] = 3'b001;test_vecs[2][1:1] = 1'b1;test_vecs[2][0:0] = 1'b0;
    test_vecs[3][4:2] = 3'b001;test_vecs[3][1:1] = 1'b0;test_vecs[3][0:0] = 1'b1;
    test_vecs[4][4:2] = 3'b010;test_vecs[4][1:1] = 1'b1; test_vecs[4][0:0] = 1'b0;
    test_vecs[5][4:2] = 3'b010;test_vecs[5][1:1] = 1'b0;test_vecs[5][0:0] = 1'b1;
    test_vecs[6][4:2] = 3'b011;test_vecs[6][1:1] = 1'b1;test_vecs[6][0:0] = 1'b0;
    test_vecs[7][4:2] = 3'b011;test_vecs[7][1:1] = 1'b0; test_vecs[7][0:0] = 1'b1;
  end
  initial begin
    $monitor("Time = %0t: i1 = %b, y = %b, y0 = %b, s0 = %b, cout = %b", $time, i1, y,y0,s0, cout);
  end
  initial {i1, y, y0} = 0;
  circuit4 circuit4_0 (i1,y,y0,s0, cout);
  initial begin
    for(i=0;i<`TESTVECS;i=i+1)
      begin #10 {i1,y,y0}=test_vecs[i];
      end
  end
end
endmodule
```

## II. Verilog VVP Output Screen Shot

```
Time = 0: i1 = 000, y = 0, y0 = 0, s0 = 0, cout = 0
Time = 20: i1 = 000, y = 1, y0 = 1, s0 = 1, cout = 0
Time = 30: i1 = 001, y = 1, y0 = 0, s0 = 0, cout = 0
Time = 40: i1 = 001, y = 0, y0 = 1, s0 = 1, cout = 0
Time = 50: i1 = 010, y = 1, y0 = 0, s0 = 0, cout = 0
Time = 60: i1 = 010, y = 0, y0 = 1, s0 = 1, cout = 0
Time = 70: i1 = 011, y = 1, y0 = 0, s0 = 0, cout = 0
Time = 80: i1 = 011, y = 0, y0 = 1, s0 = 1, cout = 0
Time = 90: i1 = xxx, y = x, y0 = x, s0 = x, cout = x
```

### III. GTKWAVE Screenshot

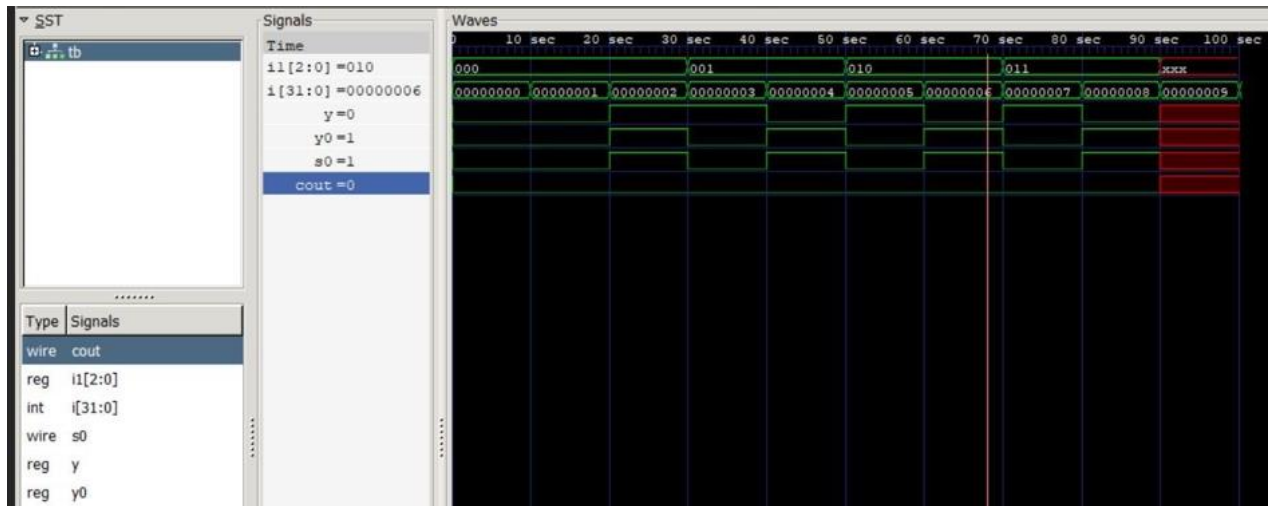

**Disclaimer:**

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.
- If found plagiarized, I will abide with the disciplinary action of the University.

Signature: Keerthan P.V.

Name: Keerthan P.V.

SRN: PES2UG23CS272

Section:3E

Date:

04/09/2024