

Digital Design and Computer Organisation Laboratory

UE23CS251A

3rd Semester, Academic Year 2024-2025

Date:12/08/2024

Name: Keerthan P.V.	SRN: PES2UG23CS272	Section E
------------------------	-----------------------	--------------

Week:1

Program Number: 1

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT AND GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE AND GATE TRUTH TABLE

I. Verilog Code Screenshot

1.and1.v

```
module and2(c,a,b);  
input a,b;  
output c;  
assign c=a&b;  
endmodule
```


2.and2_tb.v

```
module and2_test;
  reg a,b;
  wire c;
  and2 and2_test(c,a,b);
  initial
  begin
    #000 a=0;b=0;
    #100 a=0;b=1;
    #100 a=1;b=0;
    #100 a=1;b=1;
    #100;
  end
  initial
  begin
    $monitor($time,"a=%b,b=%b,c=%b",a,b,c);
  end
  initial
  begin
    $dumpfile("and2_test.vcd");
    $dumpvars(0,and2_test);
  end
endmodule
```

II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>vvp test
VCD info: dumpfile and2_test.vcd opened for output.
      0a=0,b=0,c=0
     100a=0,b=1,c=0
     200a=1,b=0,c=0
     300a=1,b=1,c=1
```

III. GTKWAVE Screenshot

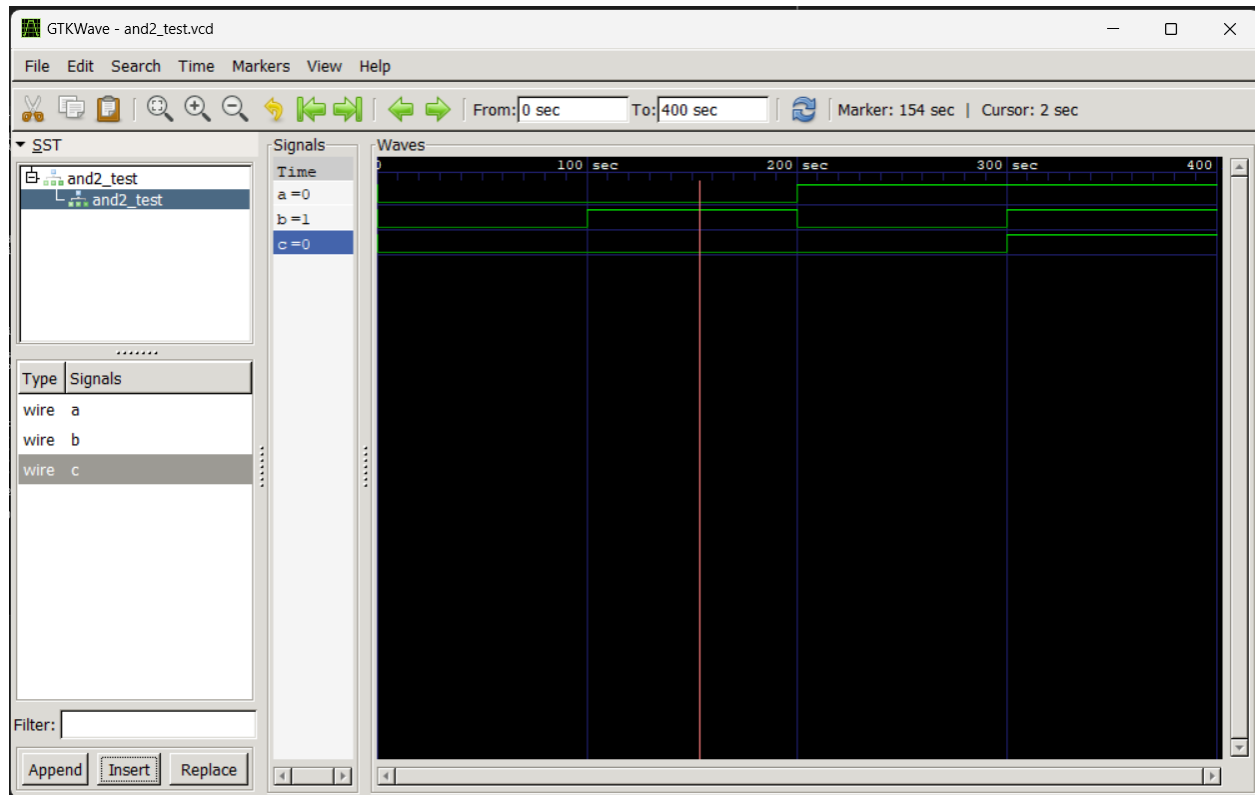

Week:1

Program Number: 2

TITLE :

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT OR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE OR GATE TRUTH TABLE

I. Verilog Code Screenshot

1.or2.v

```
module or2(c,a,b);  
input a,b;  
output c;  
assign c=a|b;  
endmodule
```


2.or2_tb.v

```
module or2_test;  
reg a,b;  
wire c;  
or2 or2_test(c,a,b);  
initial  
begin  
#000 a=0;b=0;  
#100 a=0;b=1;  
#100 a=1;b=0;  
#100 a=1;b=1;  
#100;  
end  
initial  
begin  
$monitor($time,"a=%b,b=%b,c=%b",a,b,c);  
end  
initial  
begin  
$dumpfile("or2_test.vcd");  
$dumpvars(0,or2_test);  
end  
endmodule
```

II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>vvp test
VCD info: dumpfile or2_test.vcd opened for output.
      0a=0,b=0,c=0
     100a=0,b=1,c=1
     200a=1,b=0,c=1
     300a=1,b=1,c=1
```

III. GTKWAVE Screenshot

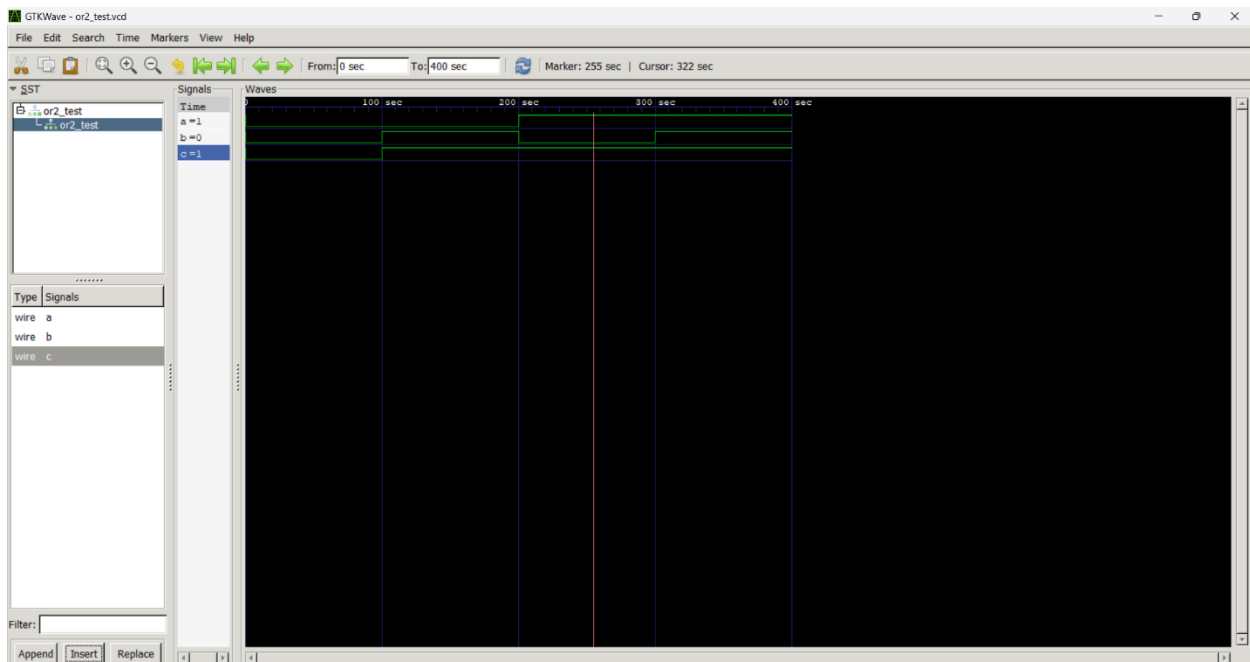

Week:1

Program Number: 3

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A NOT GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NOT GATE TRUTH TABLE

I. Verilog Code Screenshot

1.not1.v

```
module not1(a,b);  
input a;  
output b;  
assign b=!a;  
endmodule
```


2.not1_tb.v

```
module not1_test;  
reg a;  
wire b;  
not1 not1_test(a,b);  
initial  
begin  
#000 a=0;  
#100 a=1;  
#100;  
end  
initial  
begin  
$monitor($time,"a=%b, b=%b",a,b,);  
end  
initial  
begin  
$dumpfile("not1_test.vcd");  
$dumpvars(0,not1_test);  
end  
endmodule
```

II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>vvp test
VCD info: dumpfile not1_test.vcd opened for output.
          0a=0, b=1
        100a=1, b=0
```

III. GTKWAVE Screenshot

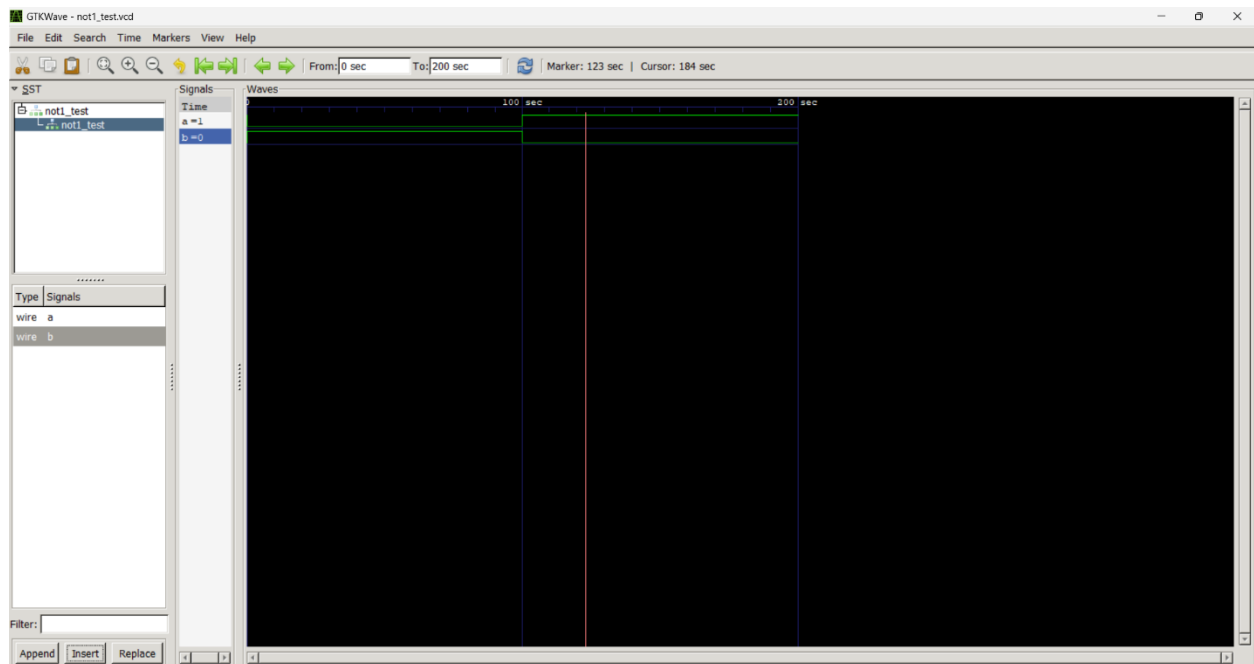

Week:1

Program Number: 4

TITLE :

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT NAND GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NAND GATE TRUTH TABLE

I. Verilog Code Screenshot

1.nand2.v

```
module nand2(c,a,b);  
input a,b;  
output c;  
assign c=!(a&b);  
endmodule
```


2.nand2_tb.v

```
module nand2_test;  
reg a,b;  
wire c;  
nand2 nand2_test(c,a,b);  
initial  
begin  
#000 a=0;b=0;  
#100 a=0;b=1;  
#100 a=1;b=0;  
#100 a=1;b=1;  
#100;  
end  
initial  
begin  
$monitor($time,"a=%b,b=%b,c=%b",a,b,c);  
end  
initial  
begin  
$dumpfile("nand2_test.vcd");  
$dumpvars(0,nand2_test);  
end  
endmodule
```


II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>vvp test
VCD info: dumpfile nand2_test.vcd opened for output.
      0a=0,b=0,c=1
     100a=0,b=1,c=1
     200a=1,b=0,c=1
     300a=1,b=1,c=0
```

III. GTKWAVE Screenshot

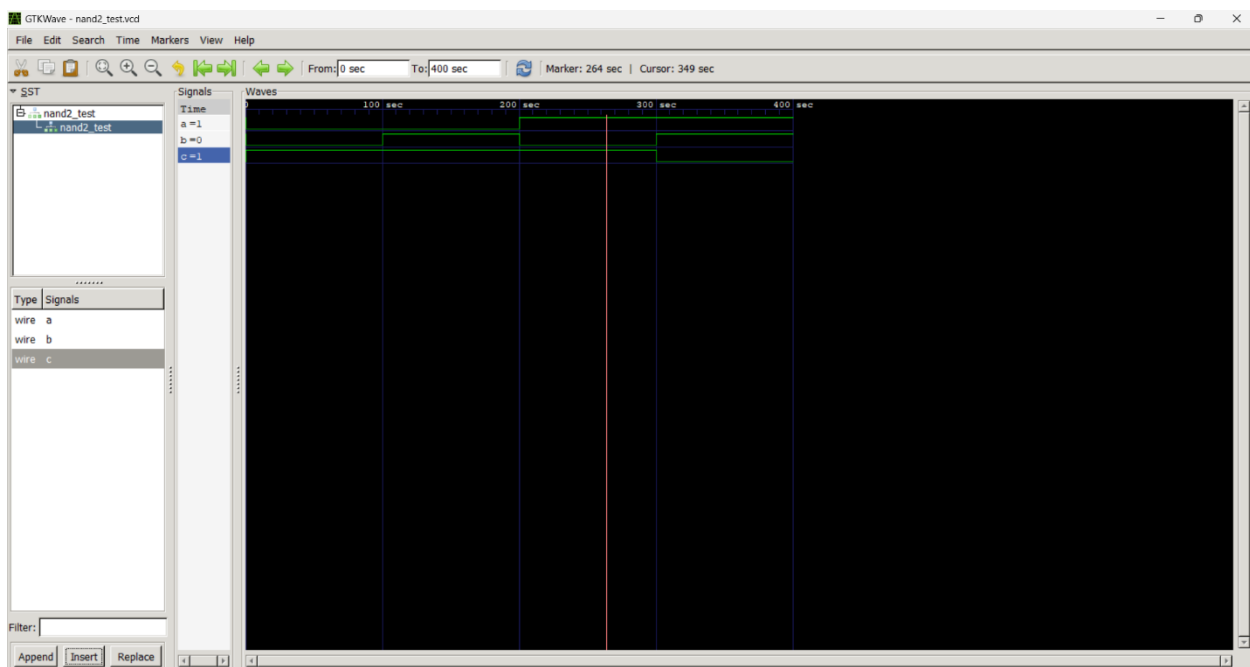

Week:1

Program Number: 5

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT NOR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE NOR GATE TRUTH TABLE

I. Verilog Code Screenshot

1.nor2.v

```
module nor2(c,a,b);  
input a,b;  
output c;  
assign c=!(a | b);  
endmodule
```


2.nor2_tb.v

```
module nor2_test;  
reg a,b;  
wire c;  
nor2 nor2_test(c,a,b);  
initial  
begin  
#000 a=0;b=0;  
#100 a=0;b=1;  
#100 a=1;b=0;  
#100 a=1;b=1;  
#100;  
end  
initial  
begin  
$monitor($time,"a=%b,b=%b,c=%b",a,b,c);  
end  
initial  
begin  
$dumpfile("nor2_test.vcd");  
$dumpvars(0,nor2_test);  
end  
endmodule
```

II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>vvp test
VCD info: dumpfile nor2_test.vcd opened for output.
      0a=0,b=0,c=1
    100a=0,b=1,c=0
    200a=1,b=0,c=0
    300a=1,b=1,c=0
```

III. GTKWAVE Screenshot

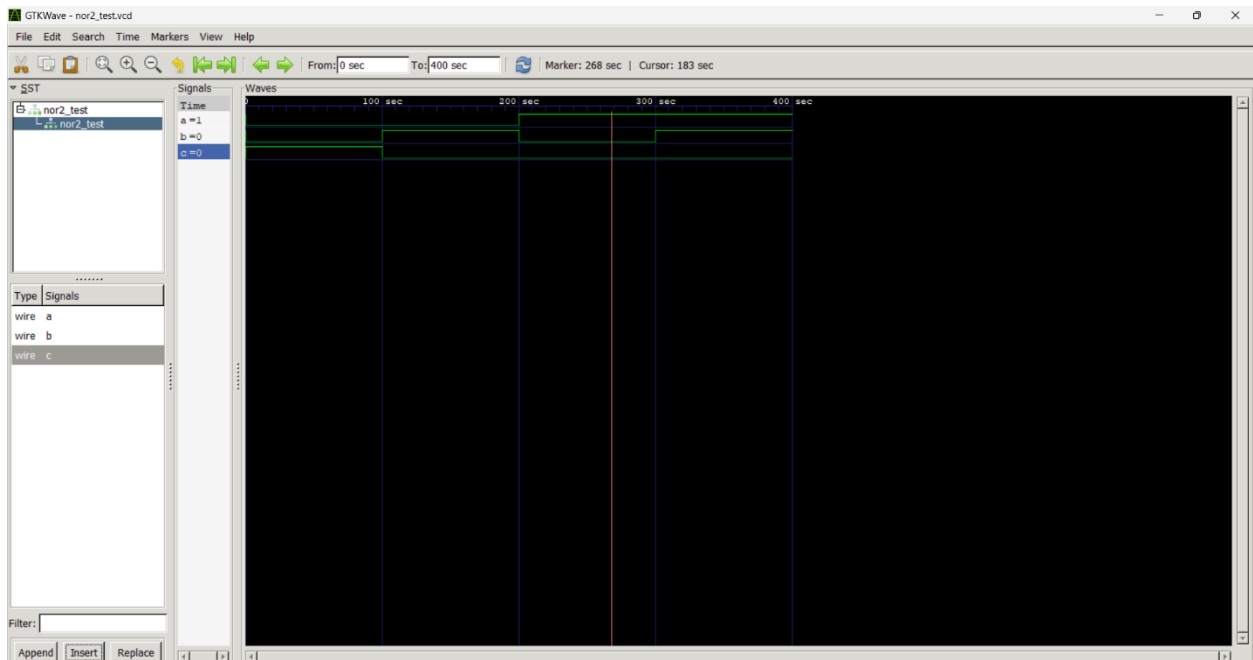

Week:1

Program Number: 6

TITLE:

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT XOR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE AND GATE TRUTH TABLE

I. Verilog Code Screenshot

1.xor2.v

```
module xor2(c,a,b);  
input a,b;  
output c;  
assign c=a^b;  
endmodule
```


2.xor2_tb.v

```
module xor2_test;  
reg a,b;  
wire c;  
xor2 xor2_test(c,a,b);  
initial  
begin  
#000 a=0;b=0;  
#100 a=0;b=1;  
#100 a=1;b=0;  
#100 a=1;b=1;  
#100;  
end  
initial  
begin  
$monitor($time,"a=%b,b=%b,c=%b",a,b,c);  
end  
initial  
begin  
$dumpfile("xor2_test.vcd");  
$dumpvars(0,xor2_test);  
end  
endmodule
```

II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>vvp test
VCD info: dumpfile xor2_test.vcd opened for output.
      0a=0,b=0,c=0
    100a=0,b=1,c=1
    200a=1,b=0,c=1
    300a=1,b=1,c=0
```

III. GTKWAVE Screenshot

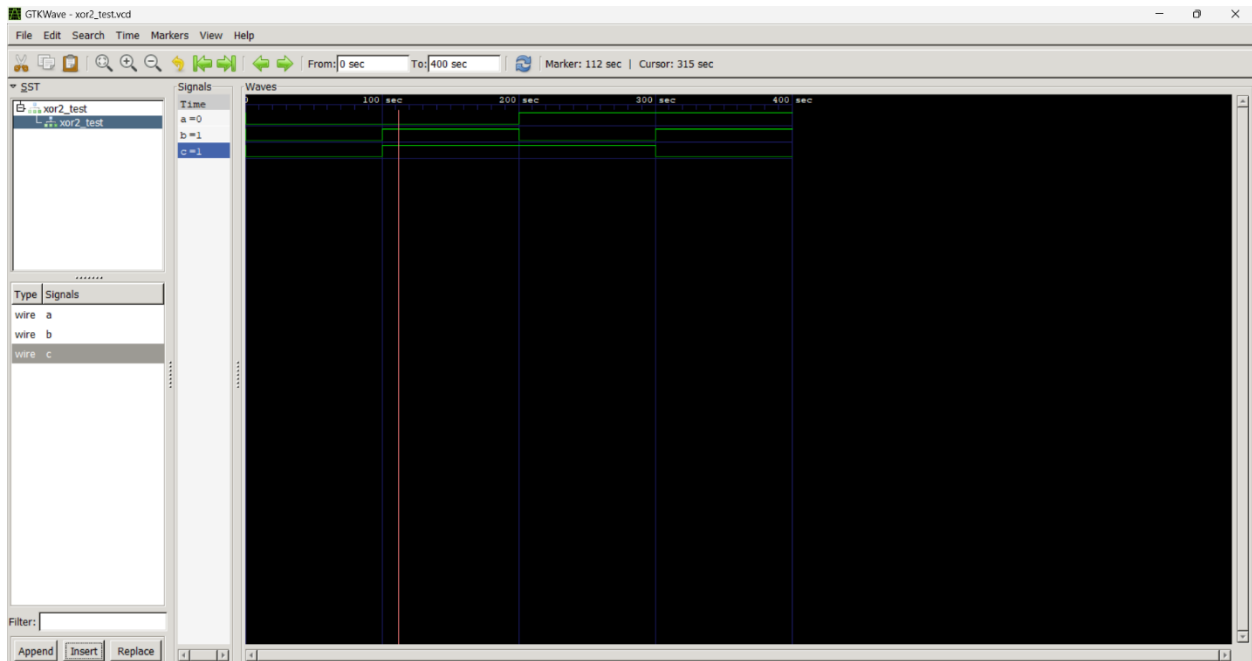

Week:1

Program Number: 7

TITLE :

WRITE A VERILOG PROGRAM TO MODEL A TWO INPUT XNOR GATE. GENERATE THE VVP OUTPUT AND SIMULATION WAVEFORM USING GTKWAVE. VERIFY THE OUTPUT AND WAVEFORM WITH THE AND GATE TRUTH TABLE

I. Verilog Code Screenshot

1.xnor2.v

```
module xnor2(c,a,b);  
input a,b;  
output c;  
assign c=!(a ^ b);  
endmodule
```


2.xnor2_tb.v

```
module xnor2_test;  
reg a,b;  
wire c;  
xnor2 xnor2_test(c,a,b);  
initial  
begin  
#000 a=0;b=0;  
#100 a=0;b=1;  
#100 a=1;b=0;  
#100 a=1;b=1;  
#100;  
end  
initial  
begin  
$monitor($time,"a=%b,b=%b,c=%b",a,b,c);  
end  
initial  
begin  
$dumpfile("xnor2_test.vcd");  
$dumpvars(0,xnor2_test);  
end  
endmodule
```

II. Verilog VVP Output Screen Shot

```
C:\iverilog\bin>vvp test
VCD info: dumpfile xnor2_test.vcd opened for output.
      0a=0,b=0,c=1
     100a=0,b=1,c=0
     200a=1,b=0,c=0
     300a=1,b=1,c=1
```

III. GTKWAVE Screenshot

 

Disclaimer:

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.
- If found plagiarized, I will abide with the disciplinary action of the University.

Signature: Keerthan P.V.

Name: Keerthan P.V.

SRN: PES2UG23CS272

Section: E

Date: 12/08/2024